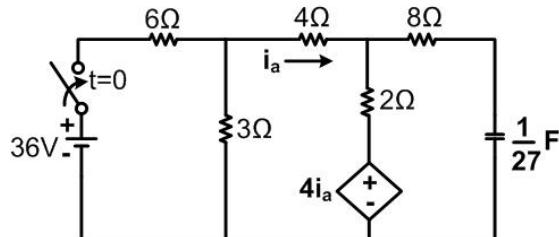
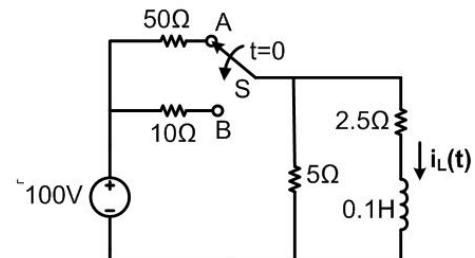
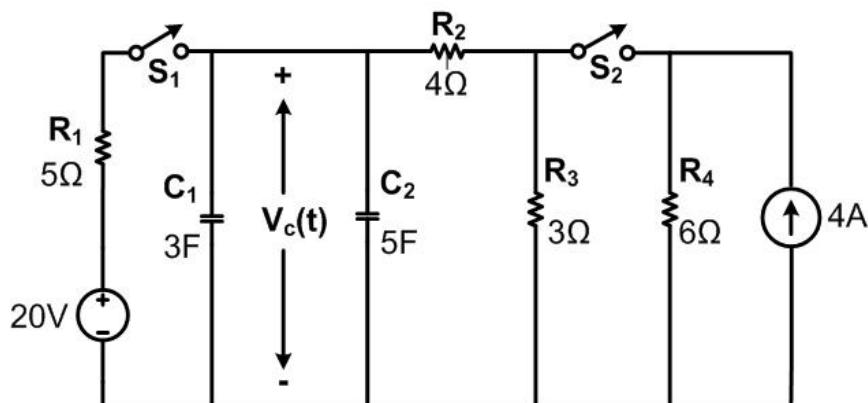


18th August, 2016**Home Assignment – 3****Transient Response**

1. For the network shown in **Fig. 1**, find the voltage across capacitor (initially uncharged) as a function of time ($t > 0$).



**Fig. 1****Fig. 2**

2. In **Fig. 2**, the switch ‘S’ was at position ‘A’ for a long time, and changes its position from ‘A’ to ‘B’ at $t = 0$. Sketch and label $i_L(t)$, and determine the time when it becomes equal to 5 A.
3. In **Fig. 3**, the switch ‘ S_1 ’ was open and ‘ S_2 ’ was closed for a long time. At $t = 0$, ‘ S_1 ’ is closed and ‘ S_2 ’ is opened simultaneously. Determine $V_c(t)$ for $t = 0, \tau, 2\tau, 5\tau$ and 10τ , where ‘ τ ’ is the time constant of the circuit for $t \geq 0$. Also determine the time constant ‘ τ ’.

**Fig. 3**

Sinusoidal Response



4. For the circuit shown in **Fig. 4**, determine the voltage ' v_c '. Assume $\omega = 10,000$ rad/s.

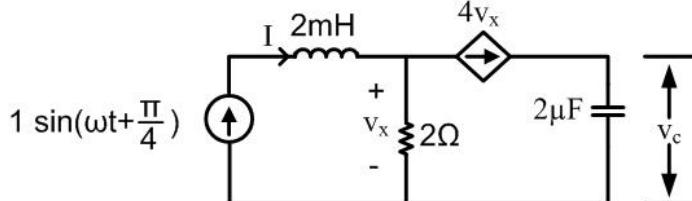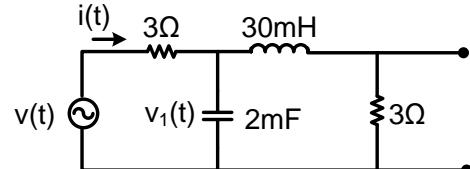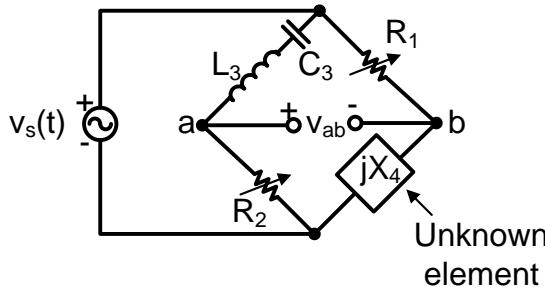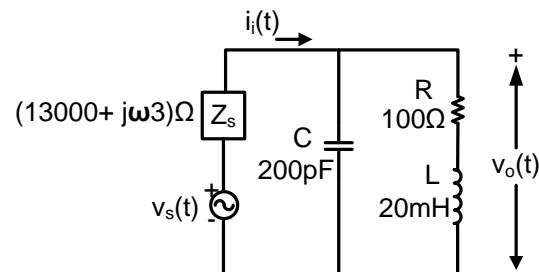**Fig. 4****Fig. 5**


5. The circuit shown in **Fig. 5** is operating in the sinusoidal steady state. The voltage across the capacitor is given by $v_1(t) = 5 \angle 23.13^\circ$ V at $\omega = 200$ rad/s. Determine $i(t)$ and $v(t)$.

6. The circuit shown in **Fig. 6**, is a Wheatstone bridge that is used to find the reactance of an unknown element (L or C). The circuit is adjusted by changing R_1 and R_2 until $v_{ab} = 0$.

- Assuming that the circuit is balanced (i.e., $v_{ab} = 0$), determine X_4 in terms of the circuit elements.
- If $C_3 = 5 \mu\text{F}$, $L_3 = 0.1 \text{ H}$, $R_1 = 100 \Omega$, $R_2 = 1 \Omega$, $v_s(t) = 24 \sin(2000t)$ V and $v_{ab} = 0$, what is the reactance of the unknown element? Is it a capacitor or an inductor? What is its value?
- Is any particular measurement frequency prohibited? Why? Justify.


**Fig. 6****Fig. 7**

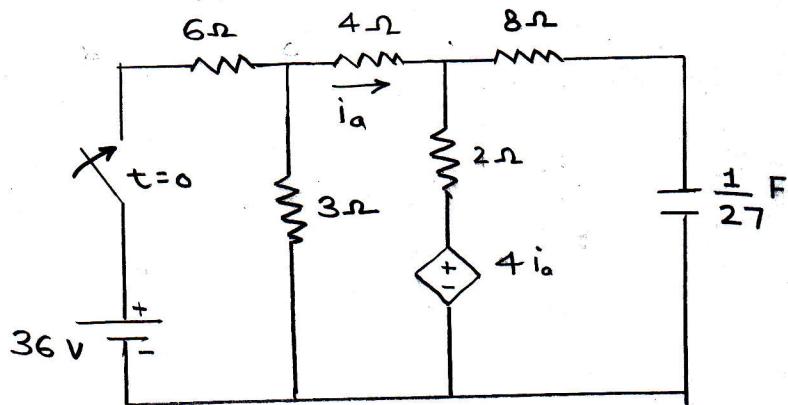7. Determine the angular frequency ' ω ' so that the current $i_l(t)$ and the voltage $v_o(t)$ in the circuit shown in **Fig. 7** are in same phase.



To find Voltage across capacitor, equivalent Thevenin network is constructed. After switch is closed.

I. Calculation of V_{Th} :-

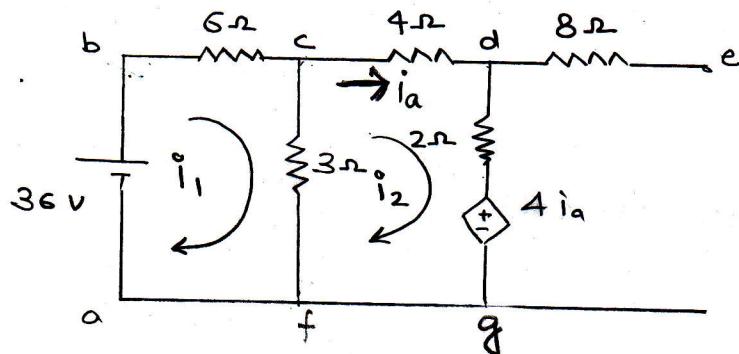

$$\text{here } i_a = i_2 \quad \text{---(i)}$$

Applying KVL in abcfa

$$-36 + 6i_1 + 3(i_1 - i_2) = 0 \Rightarrow -36 + 9i_1 - 3i_2 = 0 \quad \text{---(ii)}$$

Applying KVL in fcdfg.

$$3(i_2 - i_1) + 4i_2 + 2i_2 + 4i_2 = 0$$

$$\Rightarrow 13i_2 - 3i_1 = 0 \Rightarrow i_1 = \frac{13}{3}i_2 \quad \text{---(iii)}$$

Substituting value of i_1 from (iii) into (ii)

$$\Rightarrow -36 + 9 \times \frac{13}{3}i_2 - 3i_2 = 0$$

$$\Rightarrow -36 + 39i_2 - 3i_2 = 0 \Rightarrow 36i_2 = 36$$


$$\Rightarrow i_2 = 1 \text{ A.} \quad \text{---(iv)}$$

So

$$\begin{aligned} V_{OC} &= V_{eg} = V_{dg} = 2i_2 + 4i_2 \\ &= 6i_2 \\ &= 6V \end{aligned}$$

$$\Rightarrow V_{Th} = 6V \quad -(v)$$

Calculation of R_{Th} :

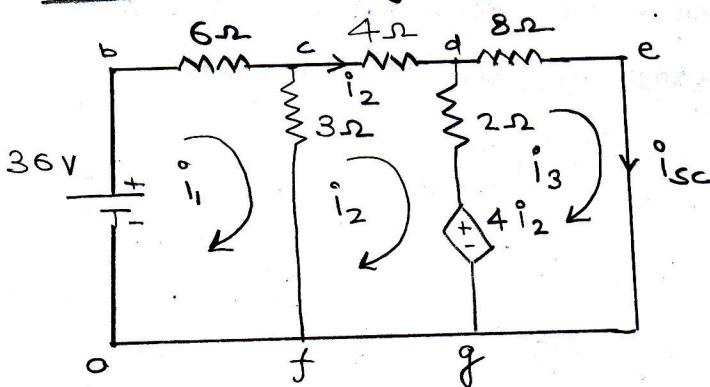

$$\text{here } i_{SC} = i_3.$$

applying KVL in loop abcfa

$$\Rightarrow -36 + 6i_1 + 3(i_1 - i_2) = 0$$

$$\Rightarrow 9i_1 - 3i_2 = 36 \Rightarrow i_1 = \frac{36 + 3i_2}{9} \quad -(vi)$$

applying KVL in loop fedgf

$$\Rightarrow 3(i_2 - i_1) + 4i_2 + 2(i_2 - i_3) + 4i_2 = 0$$

$$\Rightarrow -3i_1 + 13i_2 - 2i_3 = 0 \quad -(vii)$$

Applying KVL in loop gdeg

$$\Rightarrow -4i_2 + 2(i_3 - i_2) + 8i_3 = 0 \quad -(viii)$$

$$\Rightarrow -6i_2 + 10i_3 = 0 \Rightarrow i_3 = 0.6i_2$$

\Rightarrow on substituting the values of i_1 & i_3 from (vi) &

(viii) in eq. (vii) we obtain,

$$\Rightarrow -3 \times \left(\frac{36 + 3i_2}{9} \right) + 13i_2 - 2 \times 0.6i_2 = 0$$


$$\Rightarrow -12 - i_2 + 13i_2 - 1.2i_2 = 0$$

$$\Rightarrow 10.8i_2 = 12 \Rightarrow i_2 = \frac{12}{10.8} \text{ A.}$$

$$\text{So } i_{sc} = i_3 = 0.6 \times \frac{12}{10.8} = \frac{2}{3} \text{ A.}$$

$$\Rightarrow R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{6 \times 3}{2} = 9 \Omega.$$

So Thevenin equivalent circuit is:-

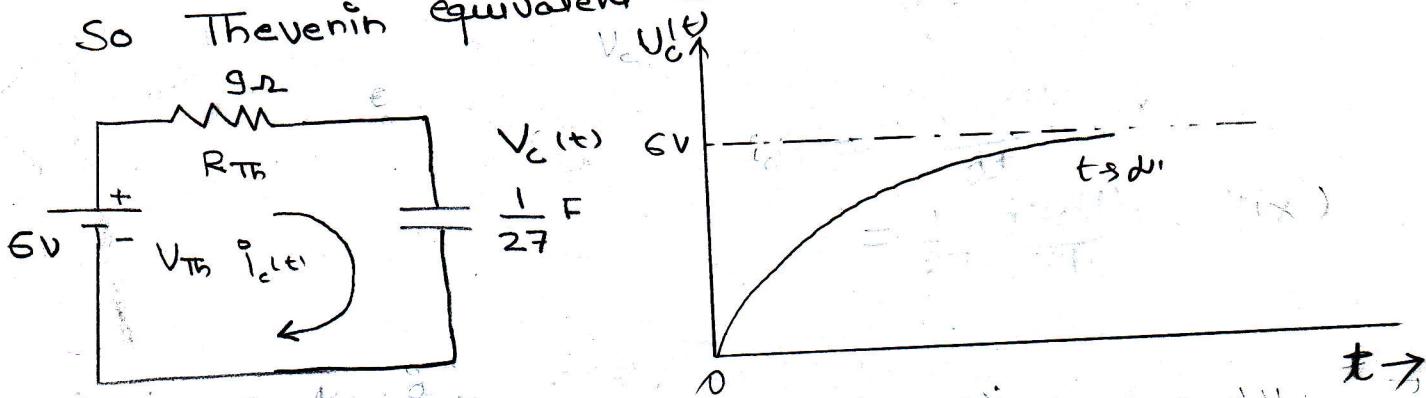

$$\therefore V_c(t) = V(\infty) + [V_{(0+)} - V(\infty)] e^{-t/\tau}$$

Since $V_{(0+)} = 0$, the value at $t=0^+$ is zero.


\therefore At $t=0^+$, capacitor is discharged, so $V_{(0+)} = 0$.

as, $t \rightarrow \infty$ capacitor is charged to 6 V. So $V(\infty) = 6 \text{ V.}$

$$\Rightarrow \text{Time Constant } \tau = RC = \frac{9}{\frac{1}{27}} = \frac{1}{3} \text{ sec}$$


$$\Rightarrow V_c(t) = 6 + [0 - 6] e^{-3t}$$

$$= 6(1 - e^{-3t}) \text{ V.}$$

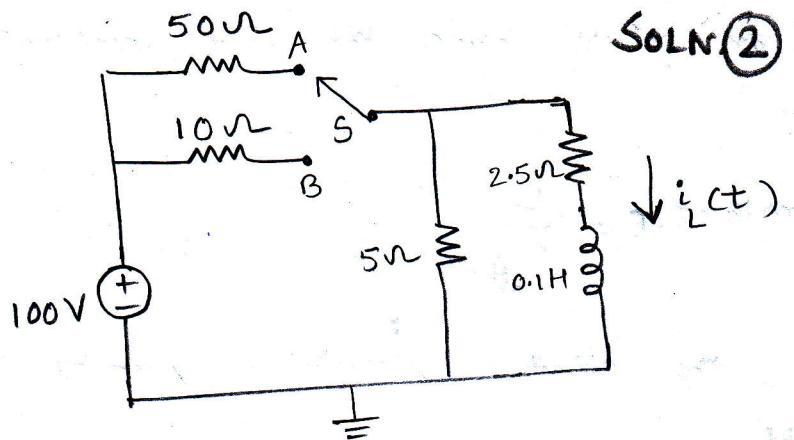

P-4

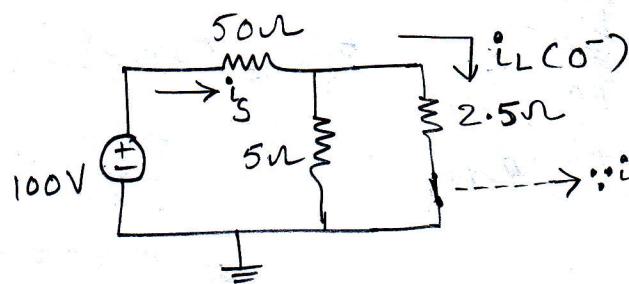* given switch 'S' was at position 'A' for a long time. Then the circuit becomes,



∴ inductor gets short circuited
when steady state has been
attained.


$i_L(0^-)$ is the initial
current through the inductor)

Then,

$$i_S = \frac{100}{50 + [5 \parallel 2.5]} = \frac{100}{50 + \left[\frac{5 \times 2.5}{5+2.5} \right]} = \frac{100}{50 + 1.666} = 1.935 \text{ A}$$

$$\therefore i_L(0^-) = i_S \times \frac{5}{5+2.5} = 1.935 \times \frac{5}{7.5} = 1.2903 \text{ A}$$

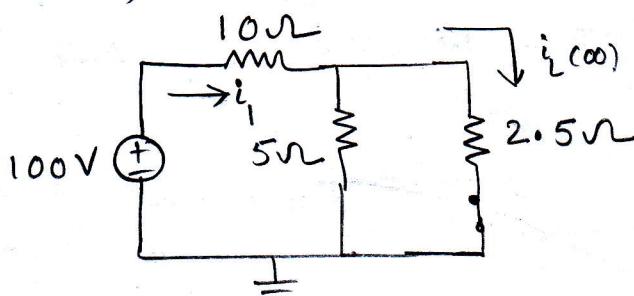* At $t=0$ switch changes from 'A' to 'B'. Then the circuit reduces to,



∴ $i_{L(\infty)}$ being final
current through
inductor)

$$\text{Then, } i_1 = \frac{100}{10 + [5 \parallel 2.5]} = \frac{100}{10 + \left[\frac{5 \times 2.5}{5+2.5} \right]} = \frac{100}{10 + 1.666} = 8.5715 \text{ A}$$


$$\text{Now, } i_L(\infty) = i_1 \times \frac{5}{5+2.5} = 8.5715 \times \frac{5}{7.5} = 5.7143 \text{ A}$$

To bind ' $i_L(t)$ ' we must have the "time-constant" of the circuit

$$\text{time-constant, } \tau = \frac{L}{R_{\text{eff}}}$$

where R_{eff} is the effective resistance seen by the inductor, $L = 0.1 \text{ H}$.

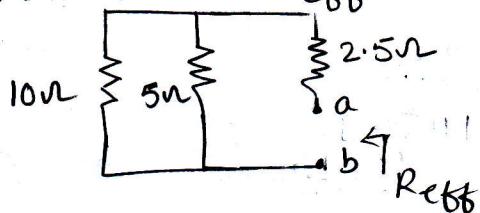To compute τ we have to determine the equivalent resistance across the inductor L . For that purpose 100 V source is short circuited and R_{eff} is determined across $a-b$.




$$\begin{aligned} R_{\text{eff}} &= [10 || 5] + 2.5 \\ &= \frac{5 \times 10}{5+10} + 2.5 \\ &= 5.833 \Omega \end{aligned}$$

$$\text{Then, } \tau = \frac{0.1 \text{ H}}{5.833 \Omega} = 17.143 \text{ ms}$$

The current through the inductor is,
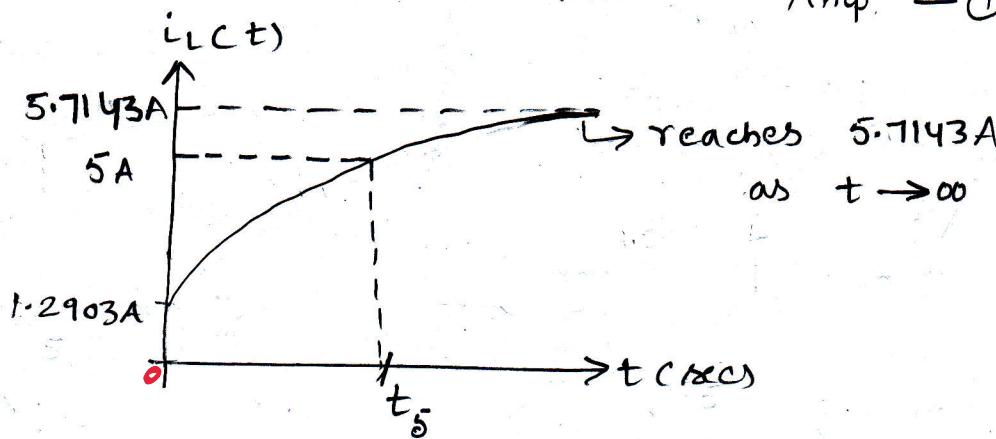
$$\begin{aligned} i_L(t) &= i_{\text{final}} + [i_{\text{initial}} - i_{\text{final}}] e^{-t/\tau} \\ &= i_{\infty} + [i(0^-) - i_{\infty}] e^{-t/\tau} \\ &= 5.7143 + [1.2903 - 5.7143] e^{-\frac{t}{0.017143}} \\ \Rightarrow i_L(t) &= 5.7143 - 4.424 e^{-58.33t} \text{ Amp. - ①} \end{aligned}$$



let t_5' be the time at which $i_L(t) = 5A$


Then from ① we can write that,

$$5 = 5.7143 - 4.424 e^{-58.33 t_5'}$$

$$\Rightarrow \frac{-58.33 t_5'}{e} = \frac{5.7143 - 5}{4.424} = 0.1614$$


$$\Rightarrow t_5' = -\frac{1}{58.33} \ln(0.1614) = 31.26 \text{ ms}$$

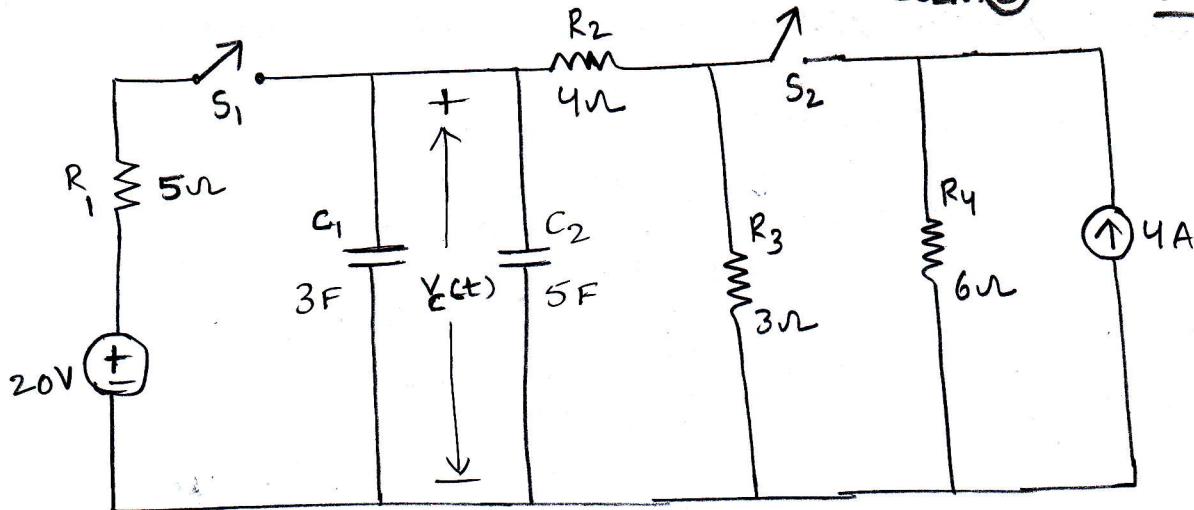∴ At $t=31.26 \text{ ms}$, current through the inductor is $5A$.



* given ' S_1 ' was open and ' S_2 ' was closed for a long time.

Then the circuit reduces to,

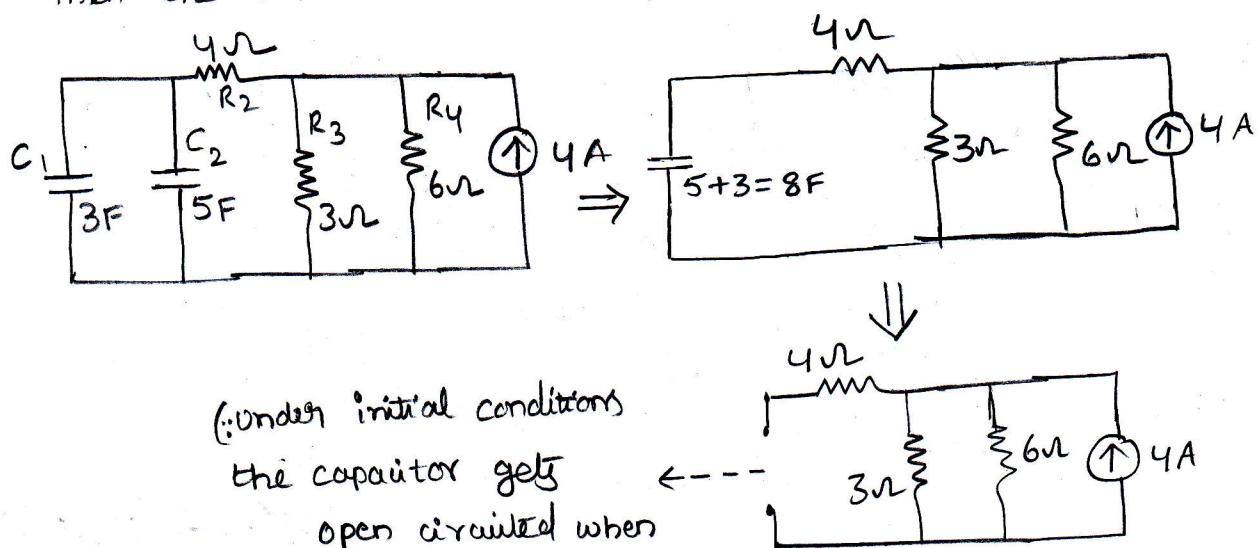

(: Under initial conditions
the capacitor gets
open circuited when
steady state is reached)


Hence,

initial voltage across the capacitors is,

$$\begin{aligned} V_c(0^-) &= 4A \times [3 \parallel 6] \Omega \\ &= 4 \times \left[\frac{3 \times 6}{3+6} \right] = 4 \times \frac{18}{9} = 8V \end{aligned}$$

* At $t=0$, ' S_1 ' is closed and ' S_2 ' is open

Then the circuit reduces to,

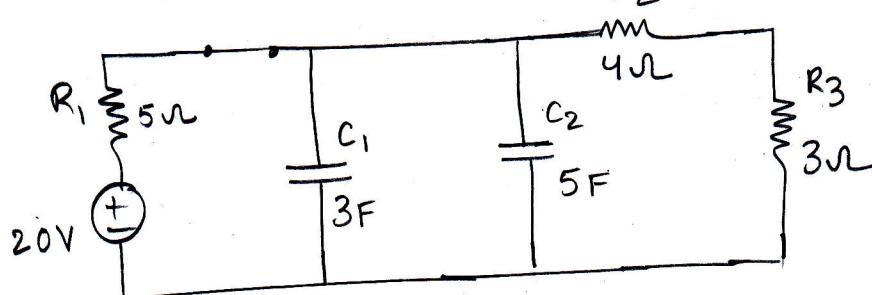

when steady state is reached, final voltage across the capacitor becomes,

$$\begin{aligned}
 V_c(\infty) &= \frac{R_2 + R_3}{R_1 + R_2 + R_3} \times 20V \\
 &= \left(\frac{4+3}{5+4+3} \right) \times 20V \\
 &= \frac{7}{12} \times 20 = 11.67V
 \end{aligned}$$

Now,

$$\begin{aligned}
 V_c(t) &= V_{\text{final}} + [V_{\text{initial}} - V_{\text{final}}] e^{-t/\tau} \\
 &= V_c(\infty) + [V_c(0^-) - V_c(\infty)] e^{-t/\tau} \\
 &= 11.67 + [8 - 11.67] e^{-t/\tau} \\
 &= 11.67 - 3.67 e^{-t/\tau} \quad \text{Volts; } \frac{1}{\tau} \text{ being time constant for } t \geq 0
 \end{aligned}$$

at $t=0$,

$$V_c(0) = 11.67 - 3.67 = 8V \quad \text{[Alternatively, } V_c(0^+) = V_c(0^-) = 8V]$$

at $t=\tau$,

$$\begin{aligned}
 V_c(\tau) &= 11.67 - 3.67 e^{-1} = 11.67 - [3.67 \times 0.3678] \\
 &= 10.319V
 \end{aligned}$$

at $t=2\tau$,

$$\begin{aligned}
 V_c(2\tau) &= 11.67 - 3.67 e^{-2} = 11.67 - [3.67 \times 0.1353] \\
 &= 11.173V
 \end{aligned}$$


at $t=5\tau$,

$$\begin{aligned}
 V_c(5\tau) &= 11.67 - 3.67 e^{-5} = 11.67 - [3.67 \times 0.00674] \\
 &= 11.645V
 \end{aligned}$$

at $t=10\tau$,

$$V_c(10\tau) = 11.67 - 3.67 e^{-10} = 11.669V$$

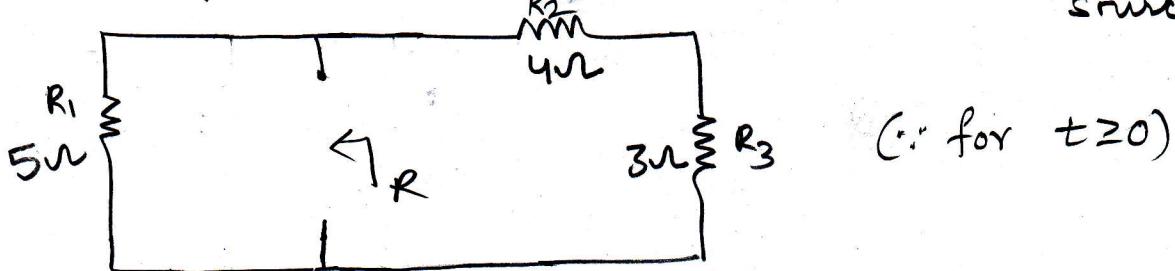To find the circuit time constant ' τ ' for $t \geq 0$,
we have to find the Thevenin equivalent resistance
across the capacitor, R by short circuiting 20V voltage source




$$R = (R_1 \parallel [R_2 + R_3])$$

$$= (5 \parallel [4+3])$$

$$= \left[\frac{5 \times 7}{5+7} \right] = \frac{35}{12}$$

$$\tau = RC = \frac{35}{12} \times 8 = \frac{280}{12} = 23.33 \text{ s}$$

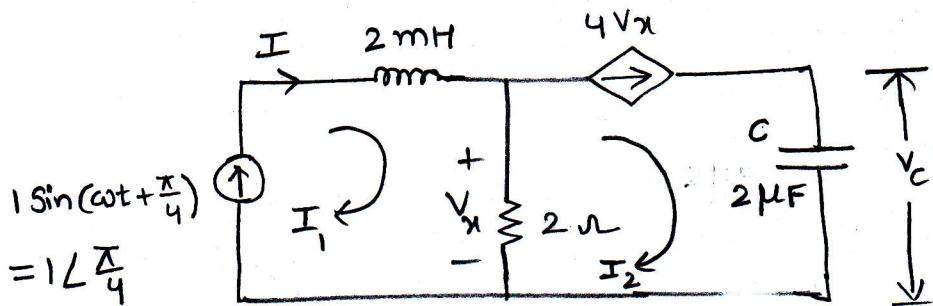\therefore b/w $t \geq 0$, circuit time constant = 23.33 sec.



$$\omega = 10,000 \text{ rad/s}$$

for the mesh currents shown in the figure, we can write,

$$I_1 = I = 1 \angle \frac{\pi}{4} \text{ Amp} \quad \text{and} \quad I_2 = 4V_x \text{ Amp}$$

where,

$$V_x = 2(I_1 - I_2) = 2\left(1 \angle \frac{\pi}{4} - 4V_x\right)$$

$$\Rightarrow V_x = 2 \angle \frac{\pi}{4} - 8V_x$$

$$\Rightarrow V_x + 8V_x = 2 \angle \frac{\pi}{4}$$

$$\Rightarrow V_x = \frac{2}{9} \angle \frac{\pi}{4} \text{ Volts}$$

Then,

$$I_2 = 4V_x = 4 \times \frac{2}{9} \angle \frac{\pi}{4} = \frac{8}{9} \angle \frac{\pi}{4} \text{ Amp}$$

NOW from the figure,

$$V_c = \frac{1}{j\omega C} \times I_2 = \frac{1}{j \times 10^4 \times 2 \times 10^{-6}} \times \frac{8}{9} \angle \frac{\pi}{4}$$

$$= \frac{8}{9} \times \frac{100}{2} \angle -\frac{\pi}{4}$$

$$= \frac{400}{9} \angle -\frac{\pi}{4} \text{ Volts}$$

$$= 44.44 \sin(\omega t - \pi/4)$$

$$= 44.44 \sin(\omega t - \pi/4) \text{ Volts}$$


$$= 44.44 \sin(\omega t - \pi/4) \text{ Volts}$$

$$= 44.44 \sin(\omega t - \pi/4) \text{ Volts}$$

$$V_1(t) = 5 \angle 23.13^\circ$$

$$\omega = 200 \text{ rad/s}$$

\therefore in loop abcd

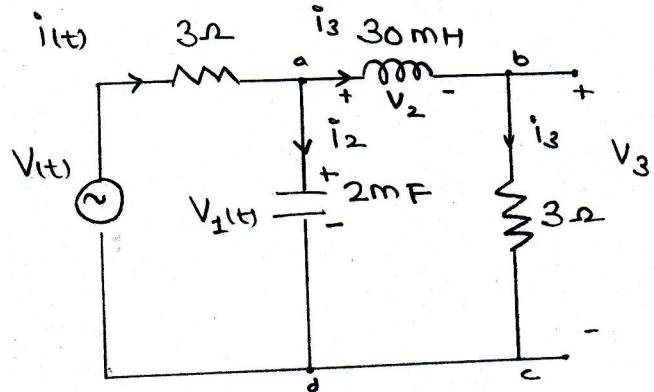

$$\Rightarrow V_1 = V_2 + V_3$$

$$V_2 = j\omega L i_3 = j6i_3 \quad ; \quad V_3 = 3i_3$$

$$\Rightarrow V_1 = i_3 (3 + j6) = 6.7 \angle 63.4^\circ i_3$$

$$\Rightarrow i_3 = \frac{5 \angle 23.13^\circ}{6.7 \angle 63.4^\circ} = 0.746 \angle -40.27^\circ \text{ A.}$$

$$\begin{aligned} \Rightarrow i_2 &= \frac{V_1}{j\omega C} = j0.4 \times 5 \angle 23.13^\circ \\ &= 2 \angle 113.13^\circ \end{aligned}$$

$$\Rightarrow i = i_2 + i_3 = 2 \angle 113.13^\circ + 0.746 \angle -40.27^\circ$$

$$\begin{aligned} i &= -0.7856 + j1.8392 + 0.568 - j0.482 \\ &= -0.2176 + j1.3572 \end{aligned}$$

$$i = 1.3745 \angle 99.1^\circ \text{ A.}$$

$$\Rightarrow V = 3i + V_1$$

$$= -0.6528 + j4.0716 + 4.598 + j1.964$$

$$= 3.9452 + j6.0356$$

$$V = 7.21 \angle 56.8^\circ \text{ V.}$$

a) ∵ circuit is balanced.


$$\text{so } V_{ab} = V_a - V_b = 0 \quad \text{---(i)}$$

$$\Rightarrow V_a = \frac{R_2 \times V_s(t)}{R_2 + j(X_{L_3} - X_{C_3})}$$

$$\text{where } X_{L_3} = \omega L_3 \quad V_s(t)$$

$$X_{C_3} = \frac{1}{\omega C_3}$$
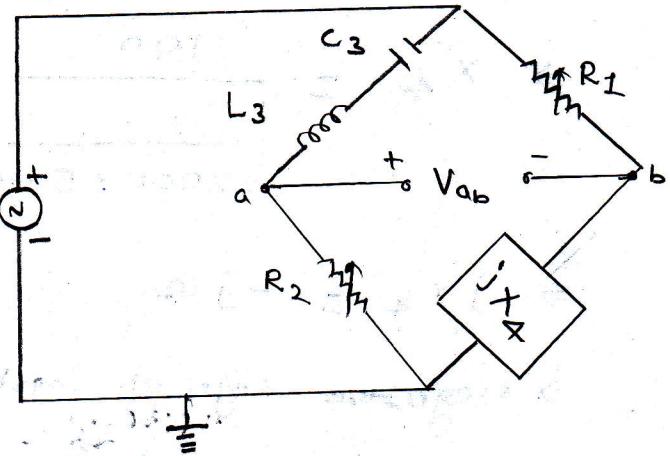
$$\Rightarrow V_b = \frac{j X_4 \times V_s(t)}{R_1 + j X_4}$$



⇒ Substituting values of V_a & V_b in eq. (i)

$$\Rightarrow \frac{R_2 \times V_s(t)}{R_2 + j(X_{L_3} - X_{C_3})} = \frac{j X_4 \times V_s(t)}{R_1 + j X_4} = 0$$

$$\Rightarrow \frac{R_2}{R_2 + j(X_{L_3} - X_{C_3})} = \frac{j X_4}{R_1 + j X_4}$$

$$\Rightarrow R_1 R_2 + j X_4 R_2 = j X_4 R_2 - X_4 (X_{L_3} - X_{C_3})$$

$$\Rightarrow R_1 R_2 = -X_4 (X_{L_3} - X_{C_3})$$

$$\Rightarrow X_4 = \frac{R_1 R_2}{(X_{C_3} - X_{L_3})}$$

$$\Rightarrow X_4 = \frac{R_1 R_2}{\left(\frac{1}{\omega C_3} - \omega L_3\right)} \quad \text{---(ii)}$$

b) $C_3 = 5 \mu F, L_3 = 0.1 H, R_1 = 100 \Omega$

$$R_2 = 1 \Omega$$

$$V_s(t) = 24 \sin(2000t) V \quad \omega = 2000 \text{ rad/s}$$

$$\Rightarrow X_4 = \frac{\frac{100}{1}}{\left(\frac{1}{2000 \times 5 \times 10^{-6}} - 2000 \times 0.1 \right)} = -1$$

$$\Rightarrow jX_4 = -j\omega$$

\Rightarrow Negative sign of impedance mean that unknown circuit element is capacitor (C)

$$\Rightarrow X_4 = \frac{1}{\omega C} \Rightarrow C = \frac{1}{X_4 \omega} = 500 \mu F$$

c) \therefore from eq i)

at particular ω' , $\omega' L_3 = \frac{1}{\omega' C_3}$ where

X_4 will be undefined.

This ω' is given by $\omega' = \frac{1}{\sqrt{L_3 C_3}}$.


$$\Rightarrow \omega' = \frac{1}{\sqrt{0.1 \times 5 \times 10^{-6}}} = 1.414 \times 10^3 \text{ rad/s}$$

\Rightarrow corresponding freq. is $f' = \frac{\omega'}{2\pi}$

$$\Rightarrow f' = 225.08 \text{ Hz}$$


SOLN. (7)

P-14

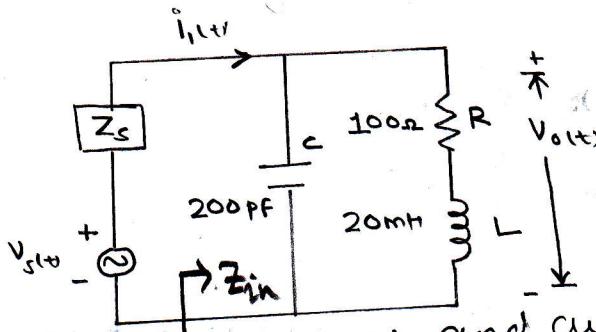

\therefore Voltage $V_o(t)$ and current $i(t)$ are in phase
Input impedance Z_{in} is purely resistive. (Note: Z_s has no role).
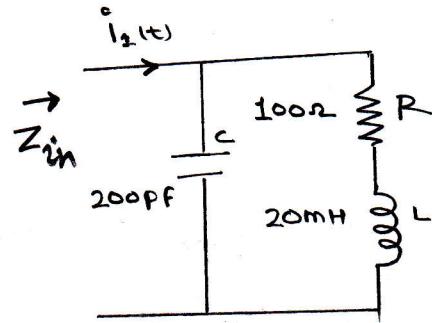
$$\begin{aligned} \Rightarrow Z_{in} &= (R + jX_L) // (-jX_C) \\ &= \frac{(R + jX_L)(-jX_C)}{(R + jX_L) - jX_C} \\ Z_{in} &= \frac{-jRX_C + X_LX_C}{R + j(X_L - X_C)} \quad \text{--- i)} \end{aligned}$$



\Rightarrow Multiplying both numerator & denominator of equation i) by $R - j(X_L - X_C)$.

$$\begin{aligned} \Rightarrow Z_{in} &= \frac{(X_LX_C - jRX_C)}{[R + j(X_L - X_C)]} \times \frac{[R - j(X_L - X_C)]}{[R - j(X_L - X_C)]} \\ &= \frac{\{RX_LX_C - RX_C(X_L - X_C)\} - j\{R^2X_C + X_LX_C(X_L - X_C)\}}{R^2 + (X_L - X_C)^2} \end{aligned}$$

$\therefore Z_{in}$ has to be purely resistive, so
imaginary part of Z should be zero.

$$\Rightarrow \frac{R^2 X_C + X_L X_C (X_L - X_C)}{R^2 + (X_L - X_C)^2} = 0$$

$$\Rightarrow R^2 X_C = X_L X_C (X_C - X_L)$$

$$\Rightarrow R^2 = X_L (X_C - X_L) [\because X_C \neq 0]$$

$$\therefore X_L = \omega L \text{ and } X_C = \frac{1}{\omega C}$$

$$\Rightarrow R^2 = \omega L \left(\frac{1}{\omega C} - \omega L \right) = \frac{L}{C} - \omega^2 L^2 \Rightarrow \omega^2 L^2 = \frac{L}{C} - R^2$$

$$\Rightarrow \omega^2 = \frac{1}{LC} - \frac{R^2}{L^2} \quad \text{--- iij}$$

on substituting $R = 100\Omega$, $L = 20\text{mH}$, $C = 200\text{pF}$

in eq. iij

$$\begin{aligned} \Rightarrow \omega &= \sqrt{\frac{1}{20\text{mH} \times 200\text{pF}} - \frac{(100\Omega)^2}{(20\text{mH})^2}} \\ &= \sqrt{\frac{1}{20 \times 10^{-3} \times 200 \times 10^{-12}} - \frac{(100)^2}{(20 \times 10^3)^2}} \\ &= \sqrt{(2.5 \times 10^{11})} = 25000000 \\ &= 499974.9994 \text{ rad/sec.} \end{aligned}$$